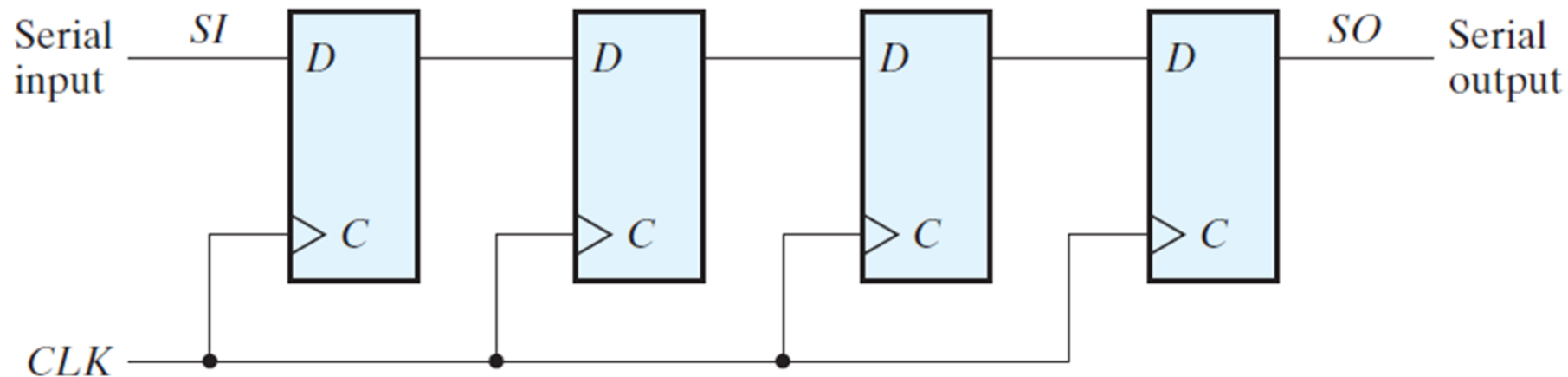


Lecture 21 – Registers and Counters 2

Chapter 6


Universal register

- If the flip-flop outputs of a shift register are accessible, then information entered serially by shifting can be taken out in parallel from the outputs of the flip-flops
- If a parallel load capability is added to a shift register, then data entered in parallel can be taken out in serial fashion by shifting the data stored in the register
- Some shift registers provide the necessary input and output terminals for parallel transfer
- They may also have both shift-right and shift-left capabilities



Universal register


- The most general shift register has the following capabilities:
 1. A *clear* control to clear the register to 0
 2. A *clock* input to synchronize the operations
 3. A *shift-right* control to enable the shift-right operation and the *serial input* and *output* lines associated with the shift right
 4. A *shift-left* control to enable the shift-left operation and the *serial input* and *output* lines associated with the shift left
 5. A *parallel-load* control to enable a parallel transfer and the n input lines associated with the parallel transfer
 6. n parallel output lines
 7. A *control state* that leaves the information in the register unchanged in response to the clock

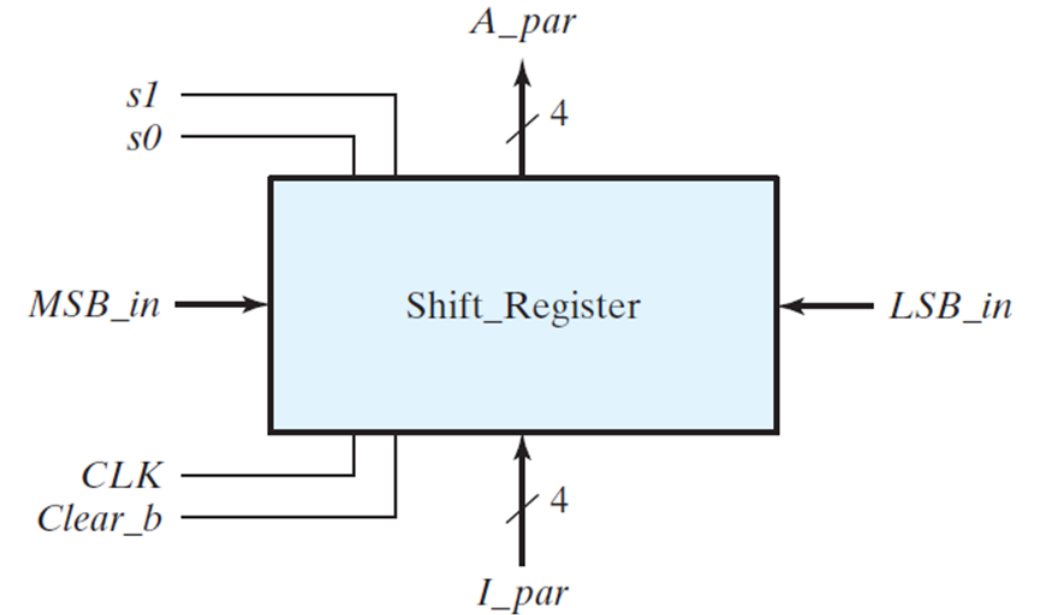

Mode Control		Register Operation
s_1	s_0	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load


Universal register

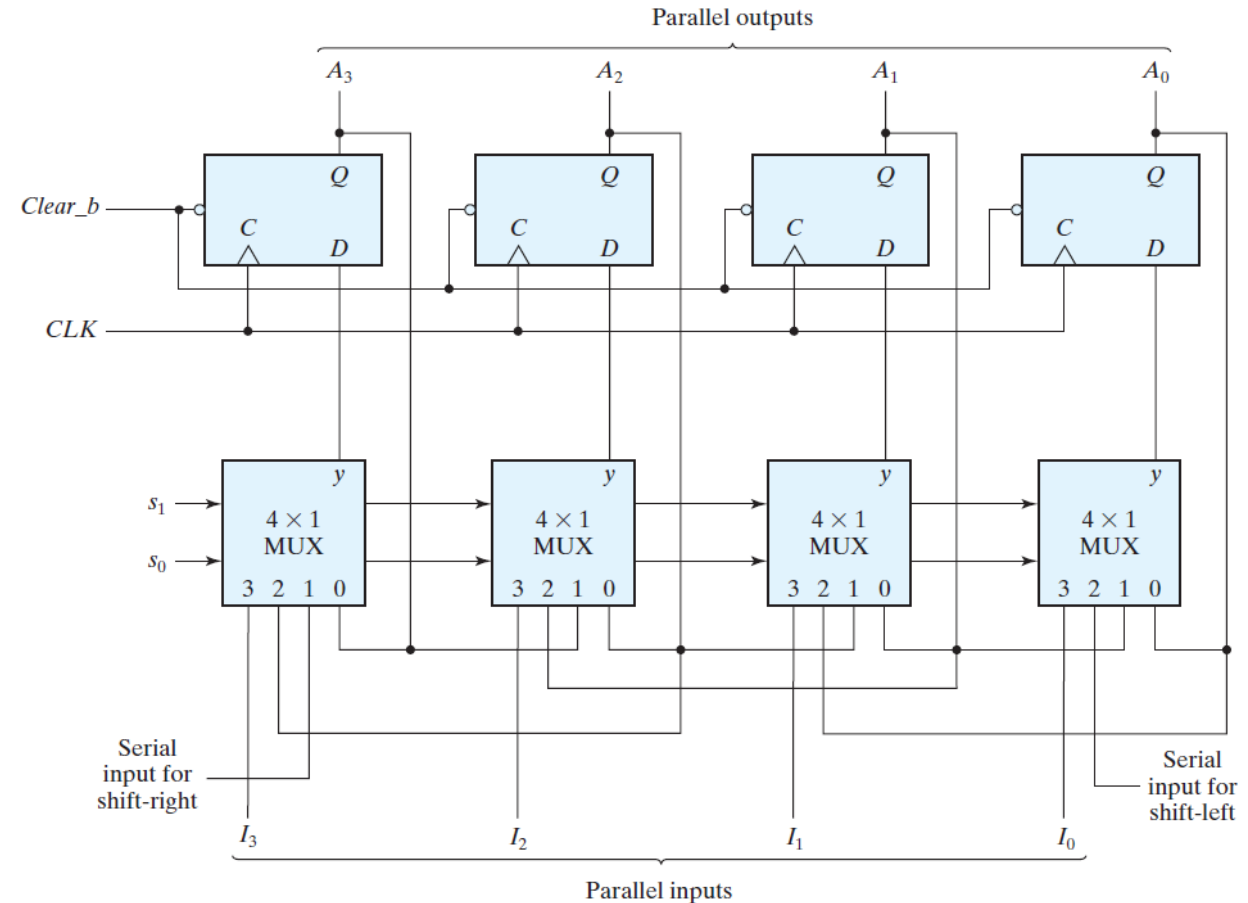- The circuit consists of four D flip-flops and four multiplexers
- The four multiplexers have two common selection inputs s_1 and s_0
- The selection inputs control the mode of operation of the register according to the function required
- The output of the MUXes are applied to the inputs of the FFs which controls the next state of the FF




Universal register

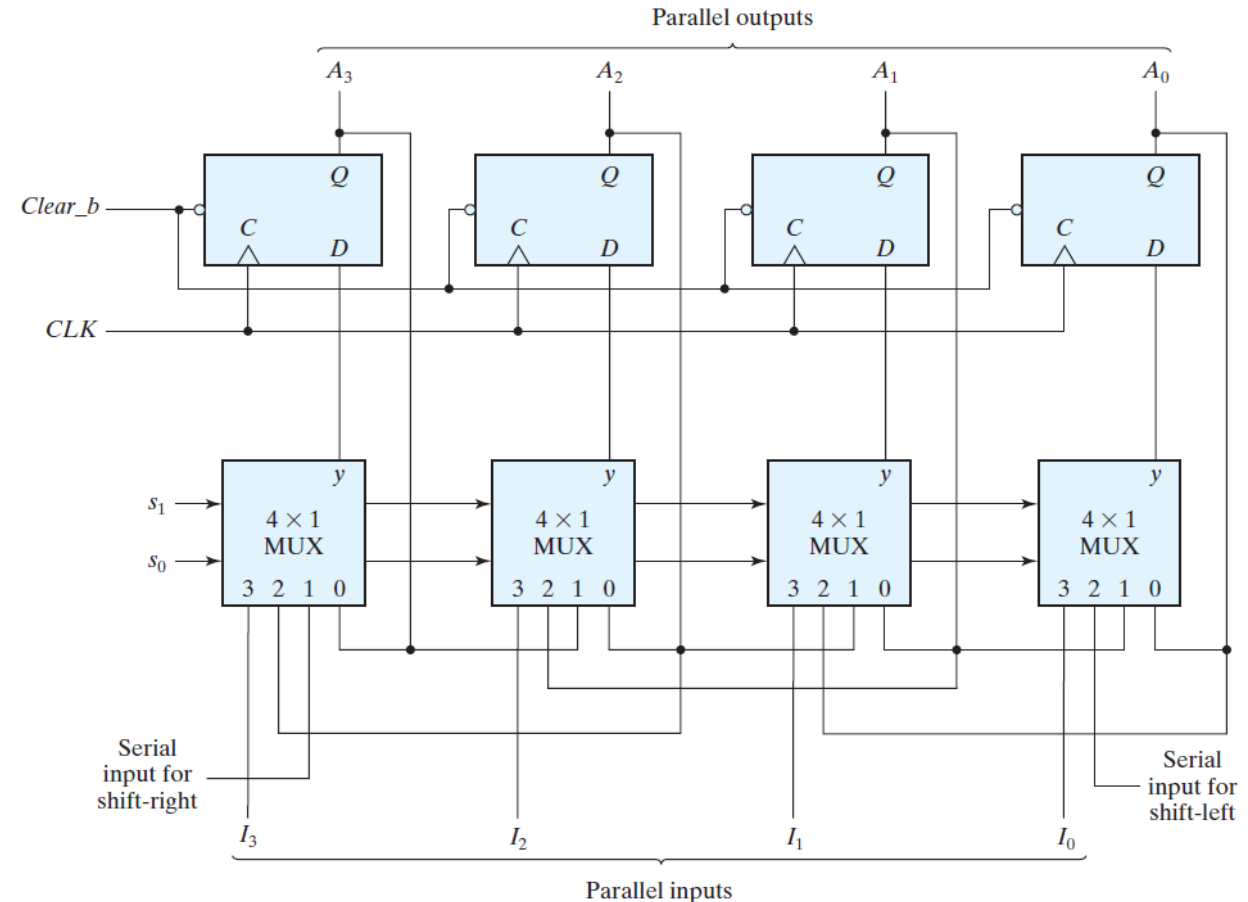- When $s_1s_0 = 00$, the present value of the register is applied to the D inputs of the flip-flops
- This condition forms a path from the output of each flip-flop into the input of the same flip-flop, so that the output recirculates to the input in this mode of operation
- The next clock edge transfers into each flip-flop the binary value it held previously, and no change of state occurs



Universal register

- When $s_1s_0 = 01$, terminal 1 of the multiplexer inputs has a path to the D inputs of the flip-flops
- This causes a shift-right operation, with the serial input transferred into flip-flop A_3
- When $s_1s_0 = 10$, a shift-left operation results, with the other serial input going into flip-flop A_0
- Finally, when $s_1s_0 = 11$, the binary information on the parallel input lines is transferred into the register simultaneously during the next clock edge

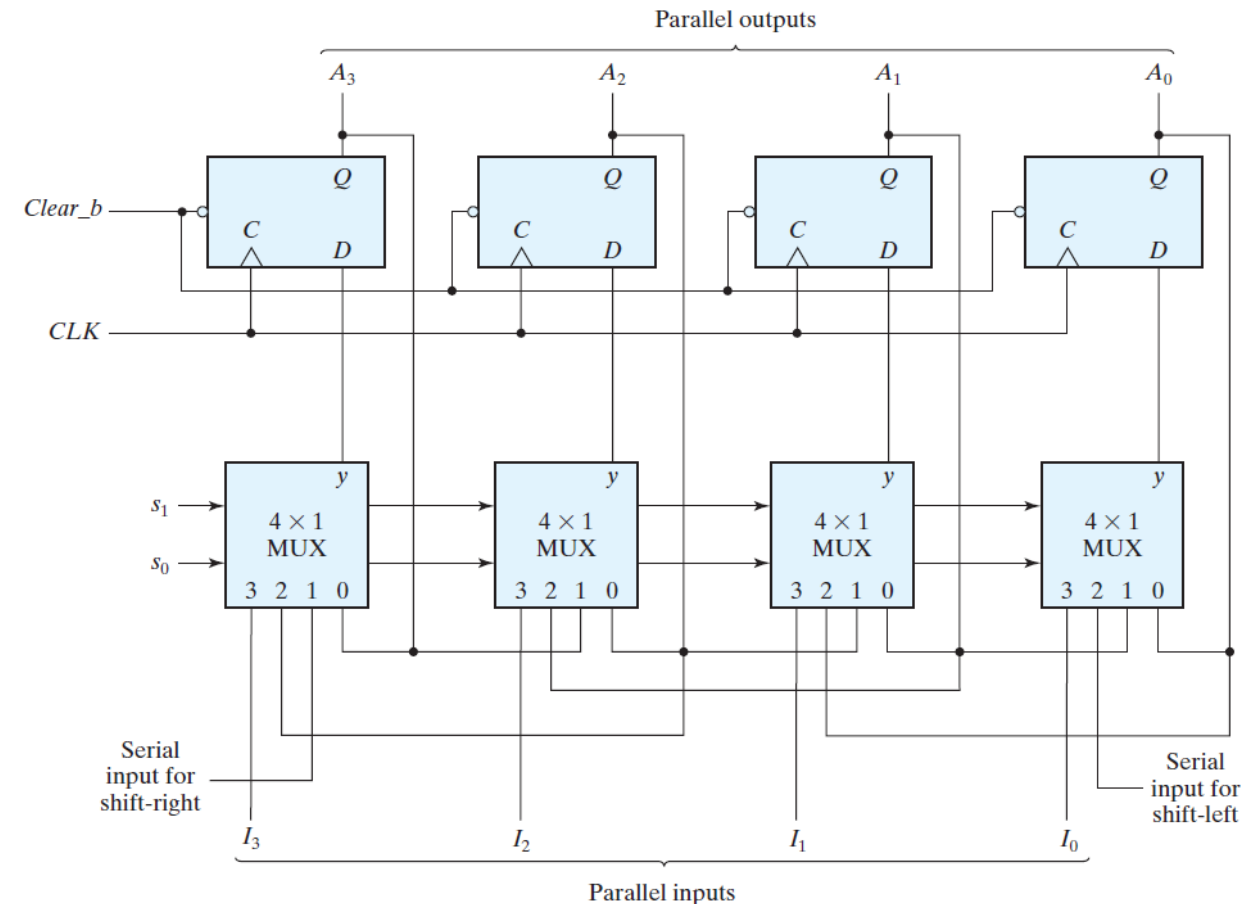


Counters

- A register that goes through a prescribed sequence of states upon the application of input pulses is called a *counter*
- The input pulses may be clock pulses, or they may originate from some external source and may occur at a fixed interval of time or at random
- The sequence of states may follow the binary number sequence or any other sequence of states
- Counters are available in two categories: **ripple counters and synchronous counters**
- In a ripple counter, a flip-flop output transition serves as a source for triggering other flip-flops
- In a synchronous counter, the C inputs of all flip-flops receive the common clock



Ripple counter - binary

- A binary ripple counter consists of a series connection of complementing flip-flops, with the output of each flip-flop connected to the C input of the next higher order flip-flop
- The flip-flop holding the least significant bit receives the incoming count pulses
- A complementing flip-flop can be obtained from a JK flip-flop with the J and K inputs tied together or from a T flip-flop
- Another possibility is to use a D flip-flop with the complement output connected to the D input
- In this way, the D input is always the complement of the present state, and the next clock pulse will cause the flip-flop to complement

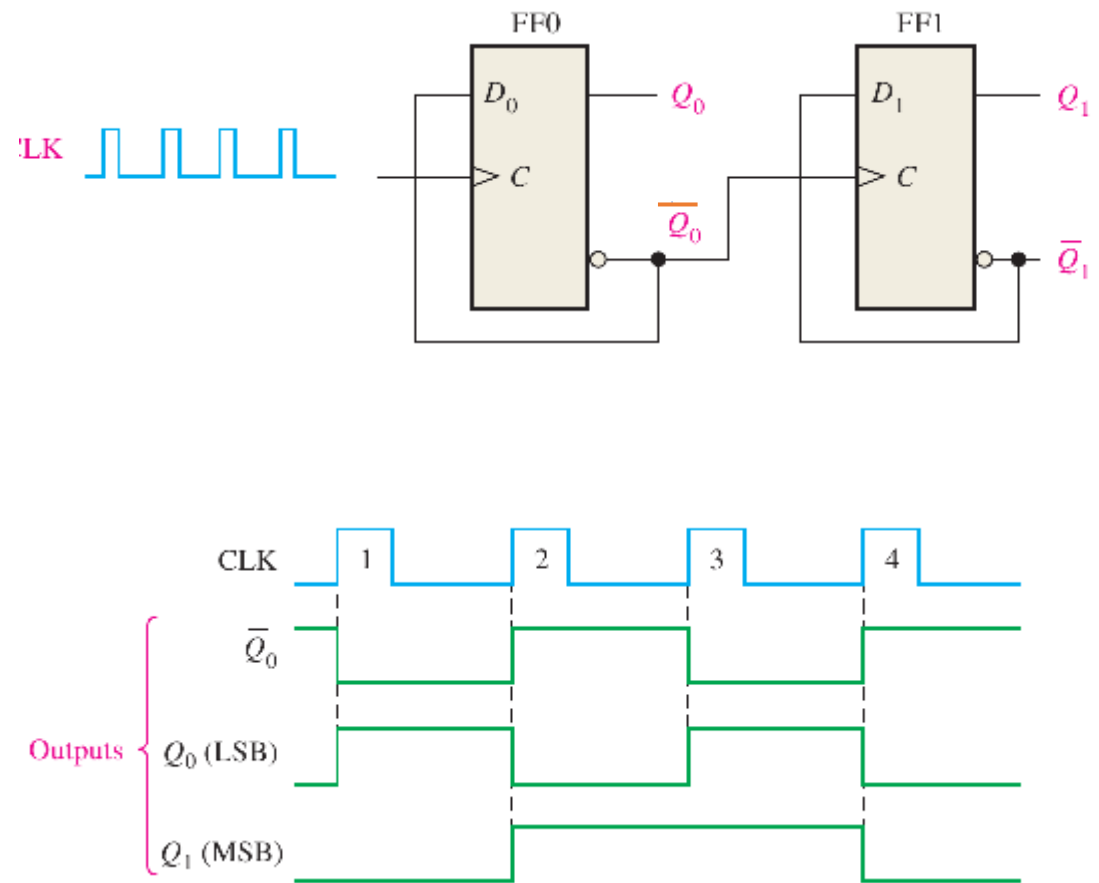



Ripple counter - binary

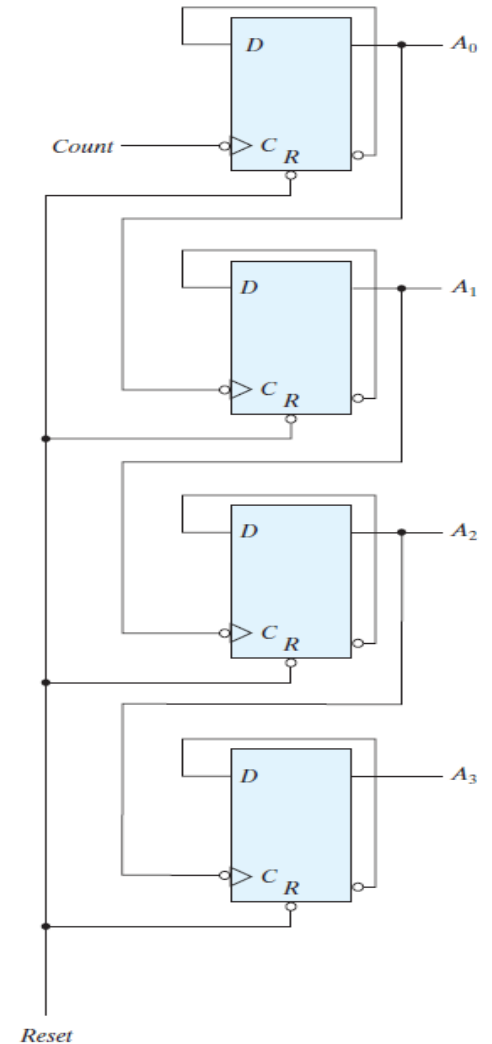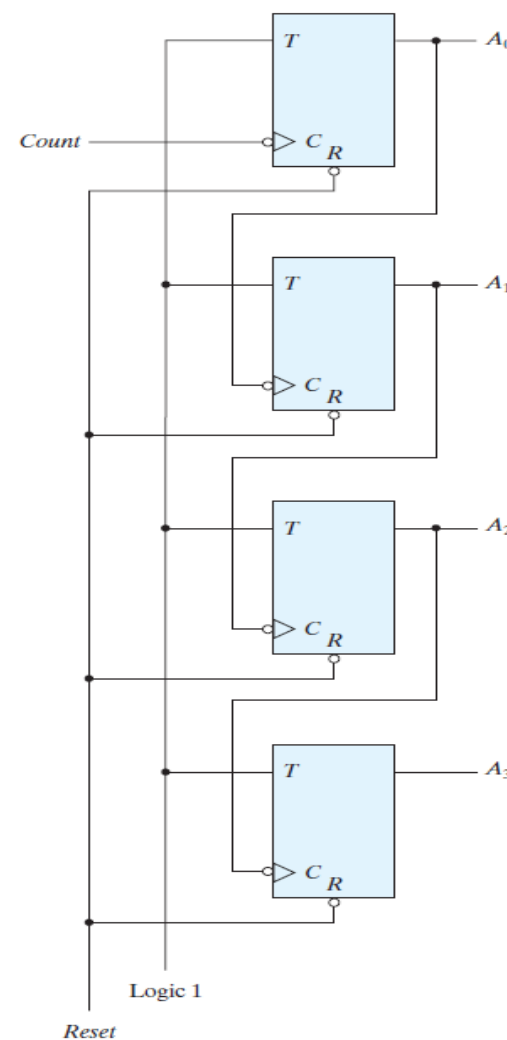- The count starts with binary 0 and increments by 1 with each count pulse input
- After the count of 15, the counter goes back to 0 to repeat the count
- The least significant bit, A_0 , is complemented with each count pulse input
- Every time that A_0 goes from 1 to 0, it complements A_1 and so on...




Ripple counter - binary

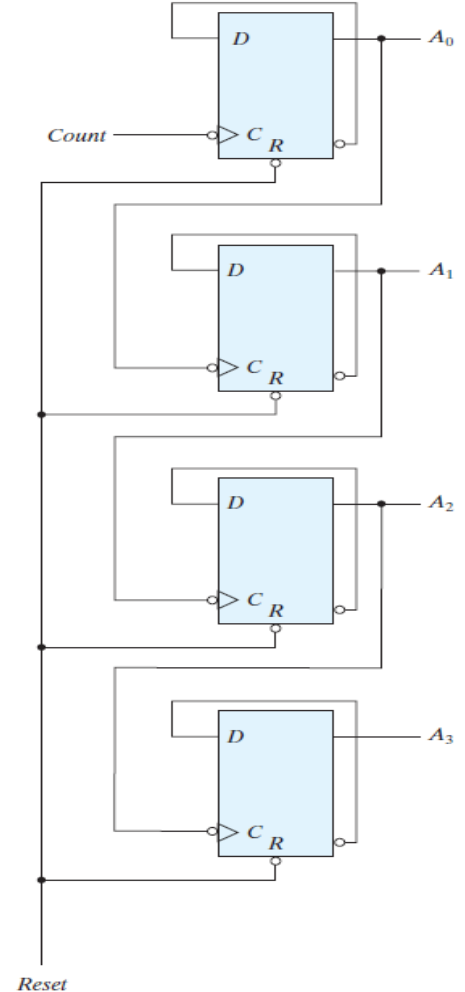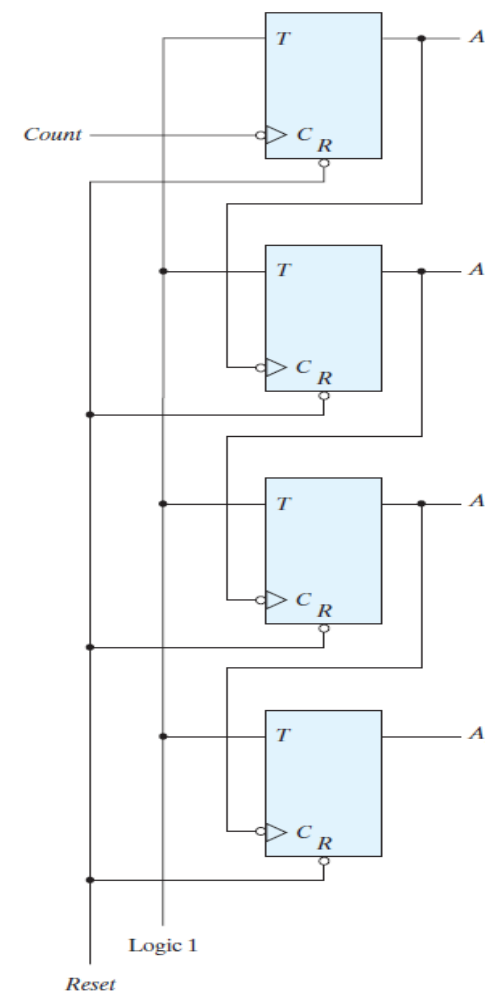- For example, consider the transition from count 0011 to 0100
- A_0 is complemented with the count pulse
- Since A_0 goes from 1 to 0, it triggers A_1 and complements it
- As a result, A_1 goes from 1 to 0, which in turn complements A_2 , changing it from 0 to 1
- A_2 does not trigger A_3 , because A_2 produces a positive transition, and the flip-flop responds only to negative transitions




Ripple counter - BCD

- A decimal counter follows a sequence of 10 states and returns to 0 after the count of 9
- Such a counter must have at least four flip-flops to represent each decimal digit, since a decimal digit is represented by a binary code with at least four bits
- The sequence of states in a decimal counter is dictated by the binary code used to represent a decimal digit
- A decimal counter is similar to a binary counter, except that the state after 1001 (the code for decimal digit 9) is 0000 (the code for decimal digit 0)

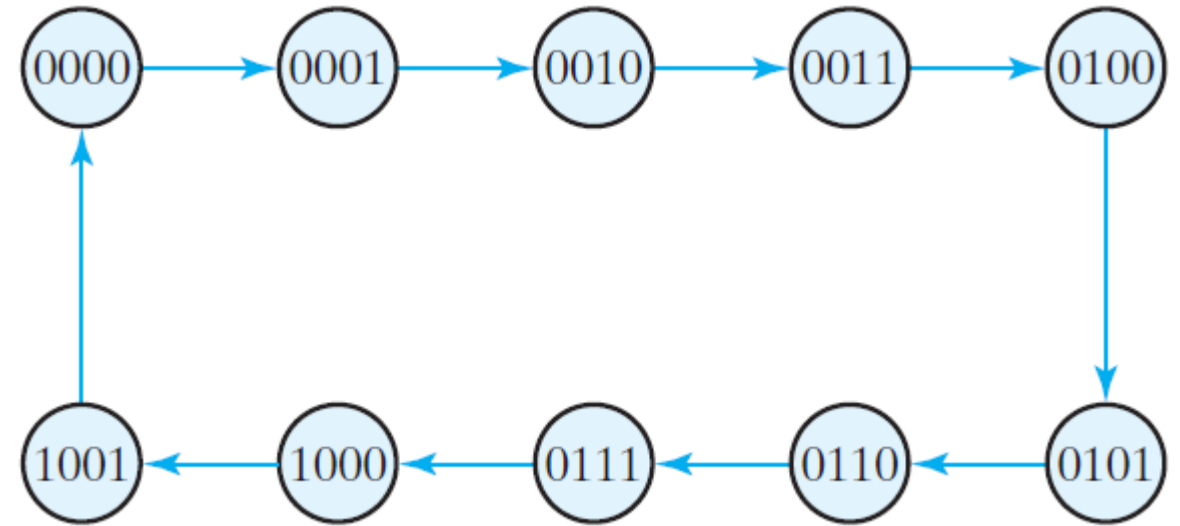

Ripple counter - BCD

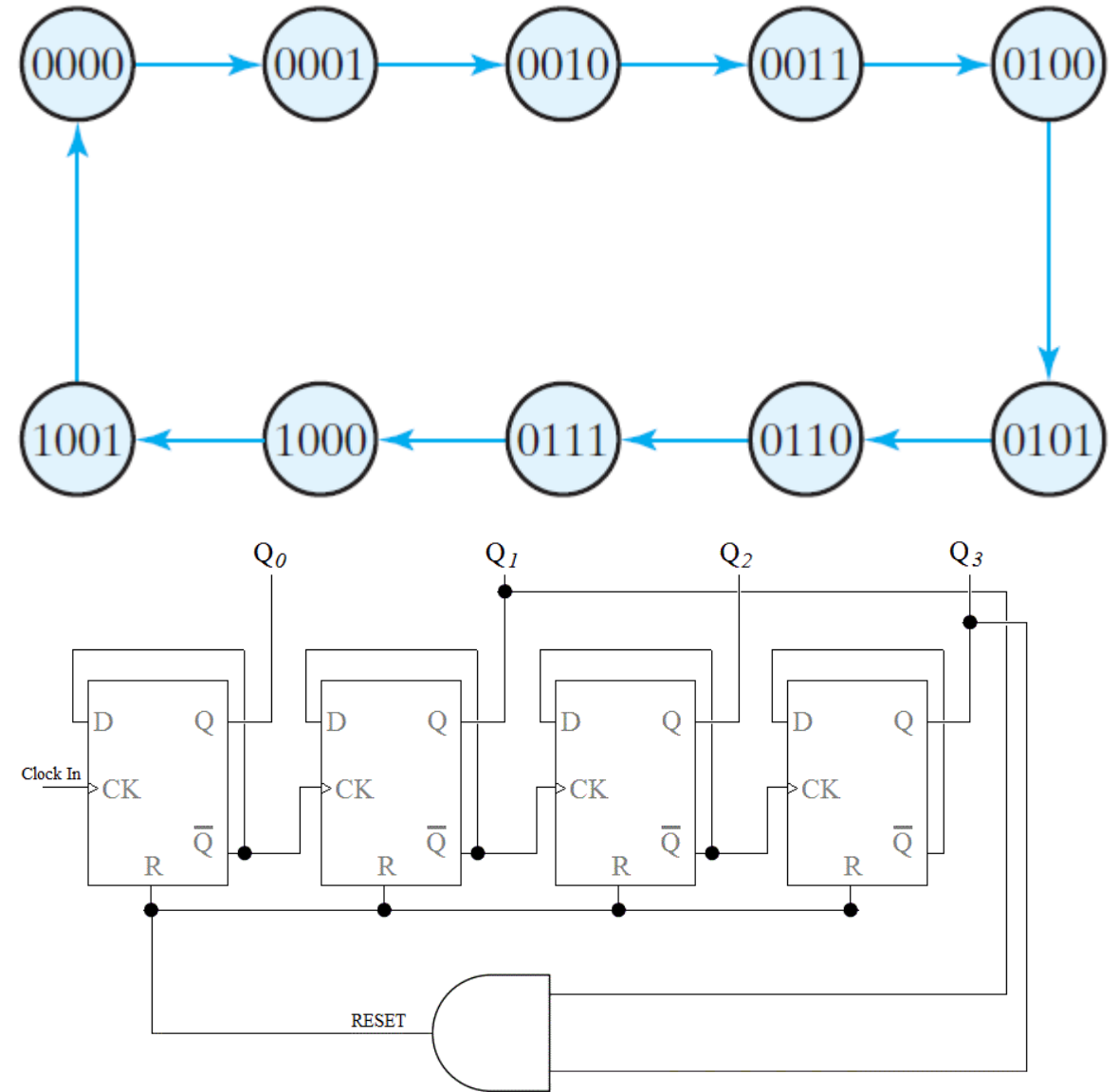- We can obtain a decade counter by clearing all the flip-flops as soon as the state 1010 is obtained
- This can be done with the asynchronous input of CLR
- The condition for 1010 is checked by ANDing Q_3 and Q_1
- This is a very commonly used counter for making clocks/timer circuits



Ripple counter - BCD

- A **decade counter** counts from 0 to 9
- To count in decimal from 0 to 99, we need a two-decade counter
- To count from 0 to 999, we need a three-decade counter
- Multiple decade counters can be constructed by connecting BCD counters in cascade, one for each decade
- The inputs to the second and third decades come from Q_8 of the previous decade
- When Q_8 in one decade goes from 1 to 0, it triggers the count for the next higher order decade while its own decade goes from 9 to 0

