


# Lecture 15 – Sequential circuits

## Chapter 5

# Binary multiplier


- The multiplicand bits are  $B_1$  and  $B_0$ , the multiplier bits are  $A_1$  and  $A_0$ , and the product is  $C_3C_2C_1C_0$

		$B_1$	$B_0$
	$A_1$	$A_0B_1$	$A_0B_0$
$A_1B_1$	$A_1B_0$		
$C_3$	$C_2$	$C_1$	$C_0$

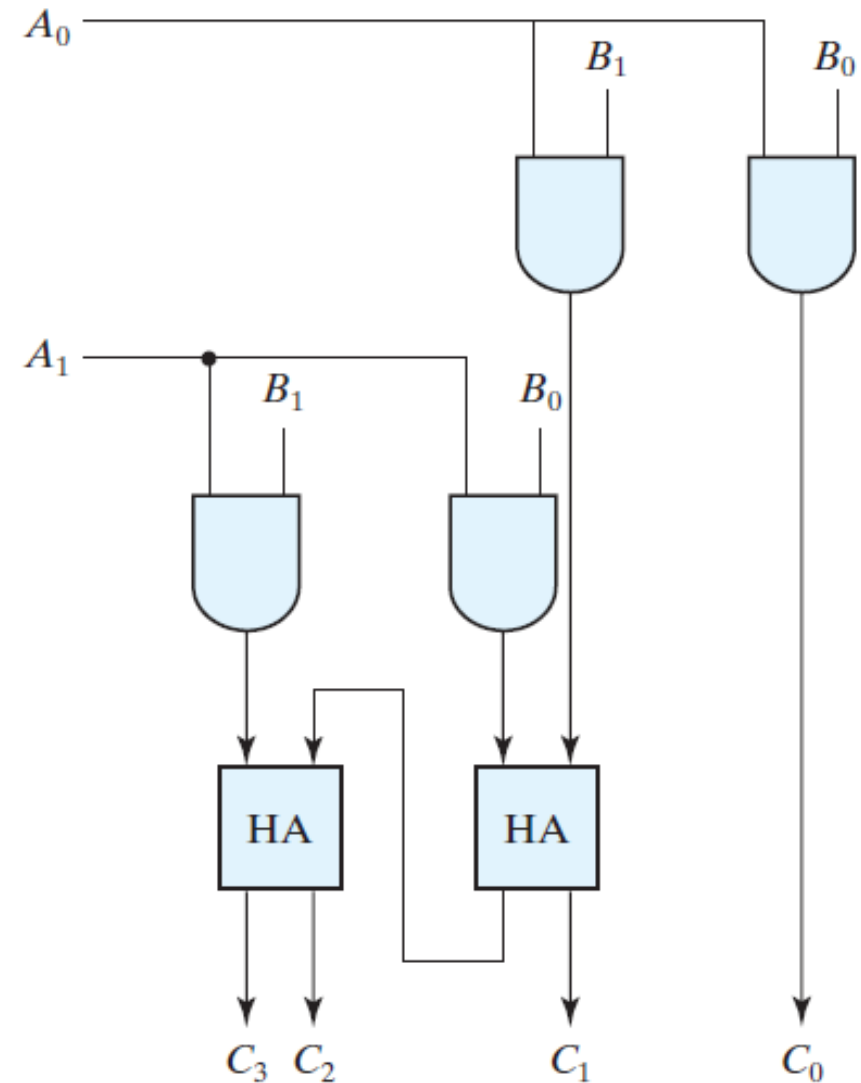
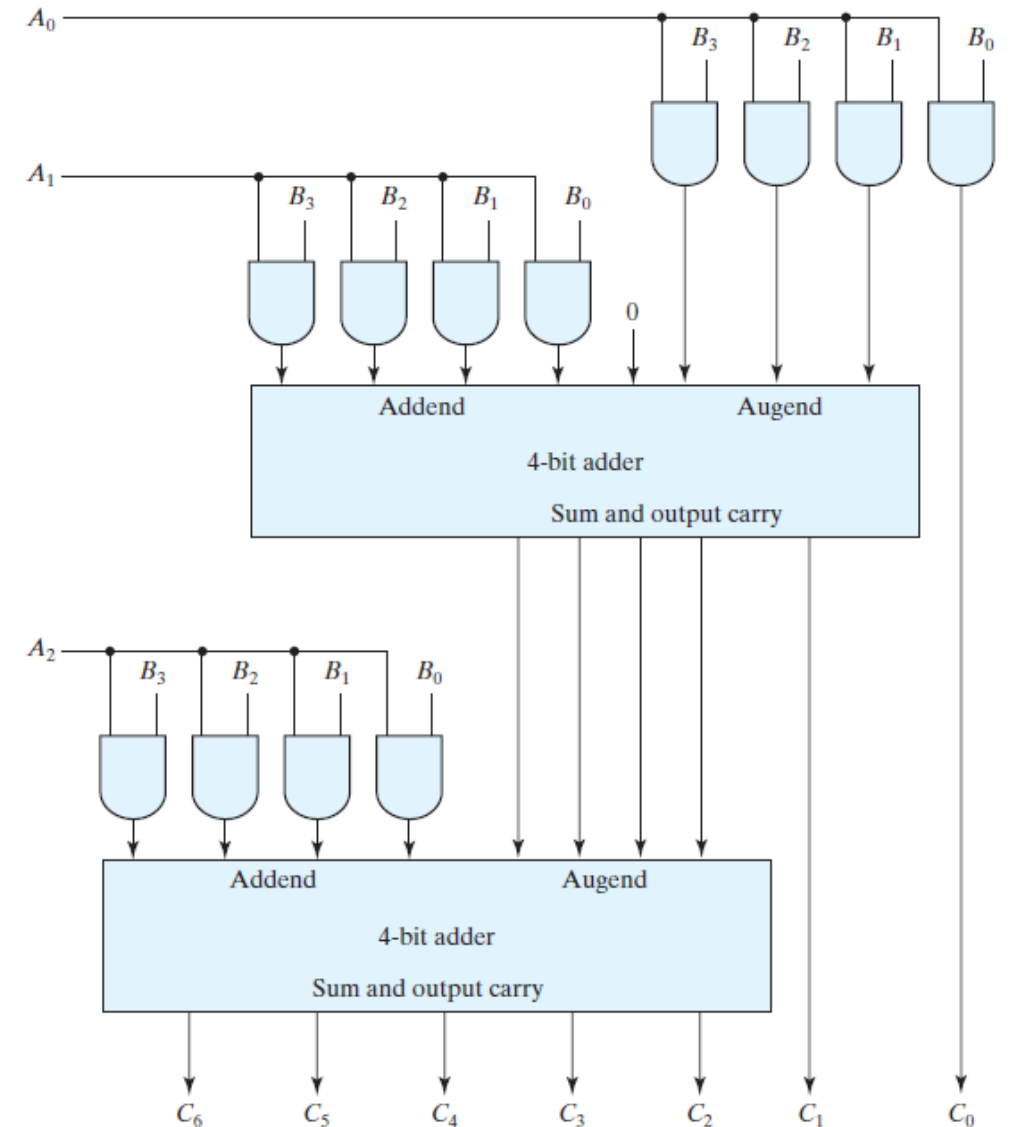
# Binary multiplier

- Let the multiplicand be represented by  $B_3B_2B_1B_0$  and the multiplier by  $A_2A_1A_0$
- combinational circuit binary multiplier with more bits can be constructed in a similar fashion
- A bit of the multiplier is ANDed with each bit of the multiplicand in as many levels as there are bits in the multiplier
- The binary output in each level of AND gates is added with the partial product of the previous level to form a new partial product
- The last level produces the product
- For  $J$  multiplier bits and  $K$  multiplicand bits, we need  $J * K$  AND gates and  $(J - 1) K$ -bit adders to produce a product of  $(J + K)$  bits



# Binary comparator


- Consider two numbers,  $A$  and  $B$ , with four digits each  $A_3A_2A_1A_0$  and  $B_3B_2B_1B_0$
- The two numbers are equal if all pairs of significant digits are equal:  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$ , **and**  $A_0 = B_0$
- To check bit-wise equality, we can use the XNOR gate

$$x_i = A_i B_i + A'_i B'_i \text{ for } i = 0, 1, 2, 3$$

- For equality to exist, all  $x_i$  variables must be equal to 1, a condition that dictates an AND operation of all variables:

$$(A = B) = x_3 x_2 x_1 x_0$$

Eg: Comparison of 2-bit numbers

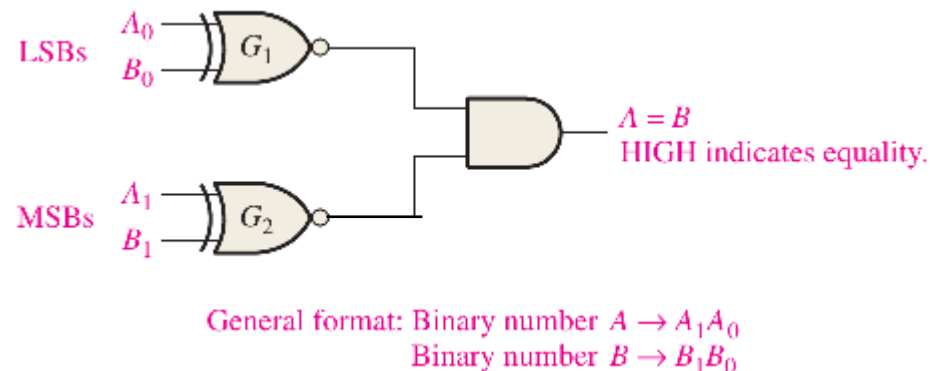




# The Binary comparator
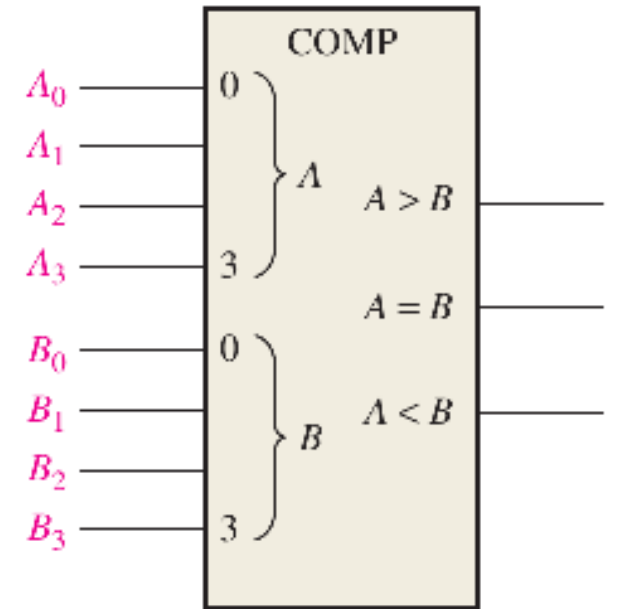
# Binary comparator

- The comparison of two numbers is an operation that determines whether one number is greater than, less than, or equal to the other number
- A *magnitude comparator* is a combinational circuit that compares two numbers  $A$  and  $B$  and determines their relative magnitudes
- The outcome of the comparison is specified by three binary variables that indicate whether  $A > B$ ,  $A = B$ , or  $A < B$
- On the one hand, the circuit for comparing two  $n$ -bit numbers has  $2^{2n}$  entries in the truth table and becomes too cumbersome, even with  $n = 3$
- On the other hand, as one may suspect, a comparator circuit possesses a certain amount of regularity



# Binary comparator

- To determine whether  $A$  is greater or less than  $B$ , we inspect the relative magnitudes of pairs of significant digits, starting from the most significant position
- If the two digits of a pair are equal, we compare the next lower significant pair of digits
- The comparison continues until a pair of unequal digits is reached
- If the corresponding digit of  $A$  is 1 and that of  $B$  is 0, we conclude that  $A > B$ . Else, we have  $A < B$

# Binary comparator

- *Eg:  $A_3 A_2 A_1 A_0 = 1001$  and  $B_3 B_2 B_1 B_0 = 1010$*
- The comparison can be expressed logically by the two Boolean functions:

$$(A > B) = A_3 B'_3 + x_3 A_2 B'_2 + x_3 x_2 A_1 B'_1 + x_3 x_2 x_1 A_0 B'_0$$

$$(A < B) = A'_3 B_3 + x_3 A'_2 B_2 + x_3 x_2 A'_1 B_1 + x_3 x_2 x_1 A'_0 B_0$$



# Binary comparator


$$x_i = A_i B_i + A'_i B'_i \text{ for } i = 0, 1, 2, 3$$

$$(A = B) = x_3 x_2 x_1 x_0$$

$$\begin{aligned} (A > B) &= A_3 B'_3 + x_3 A_2 B'_2 + x_3 x_2 A_1 B'_1 \\ &\quad + x_3 x_2 x_1 A_0 B'_0 \end{aligned}$$

$$\begin{aligned} (A < B) &= A'_3 B_3 + x_3 A'_2 B_2 + x_3 x_2 A'_1 B_1 \\ &\quad + x_3 x_2 x_1 A'_0 B_0 \end{aligned}$$

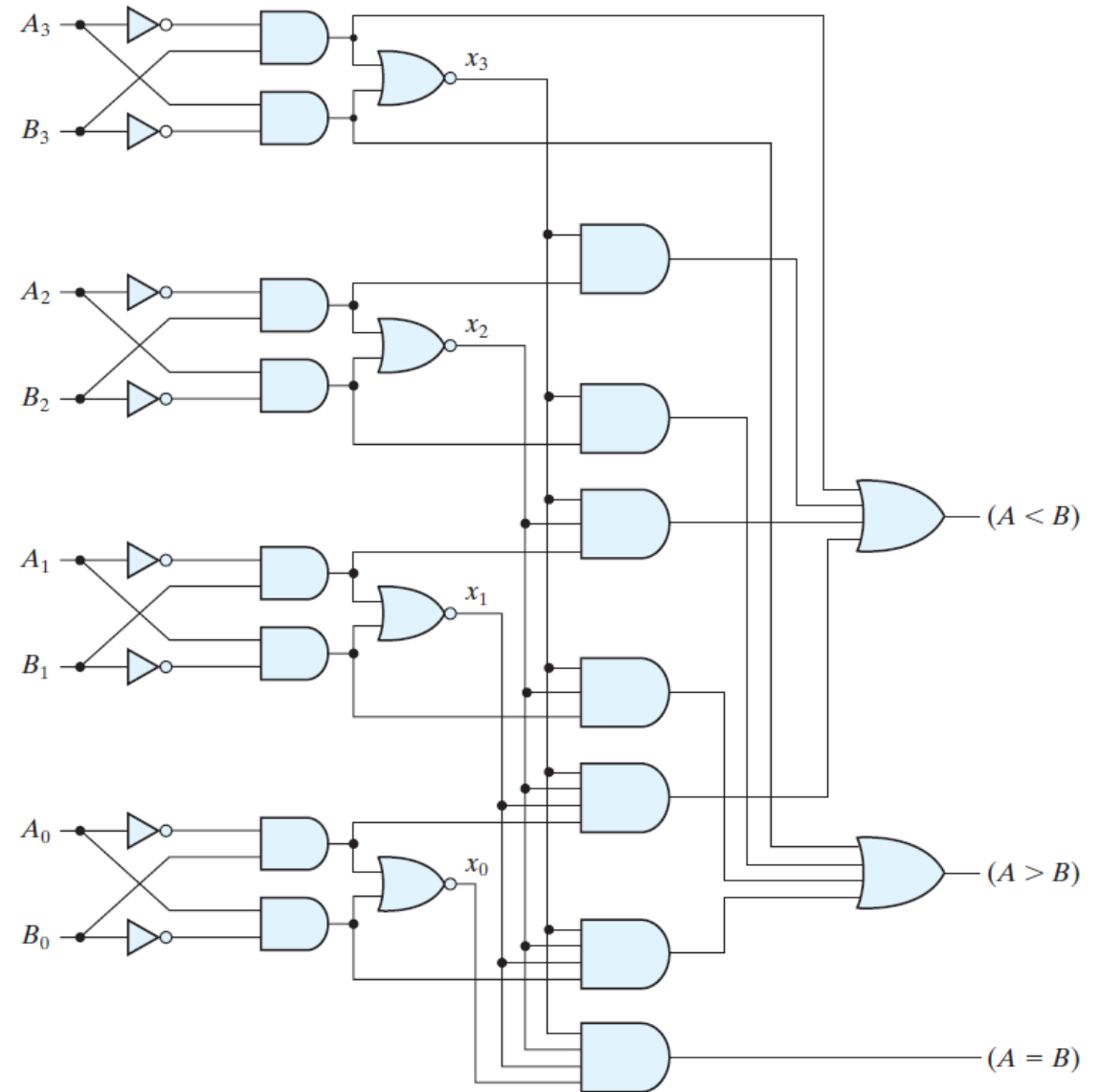Interesting: Can we prove that only one of (A=B), (A>B) and (A<B) will be “1” at any given time?





# Sequential circuits

## Chapter 5

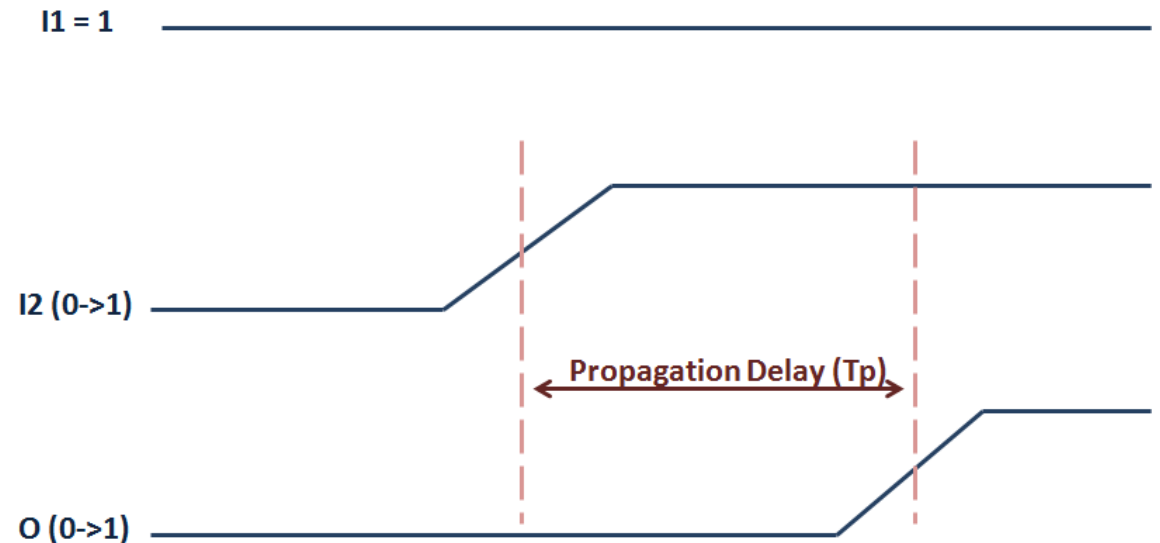
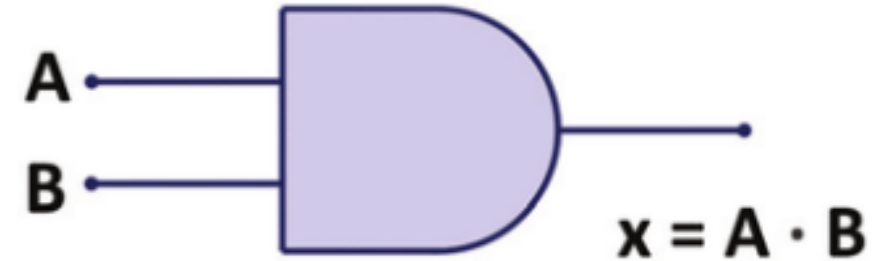
# Gate delays

- When we apply an input to a gate, the output does not change immediately – there is a delay between the input application and appearance of the correct output
- This delay is generally of the order of nanoseconds, but can add up as signal goes through multiple gates
- *While making a digital IC design, gate delay (and by extension timing) is the single biggest consideration of all time!*
- Other things to worry about are silicon real estate, power consumption, reliability, testability, etc.



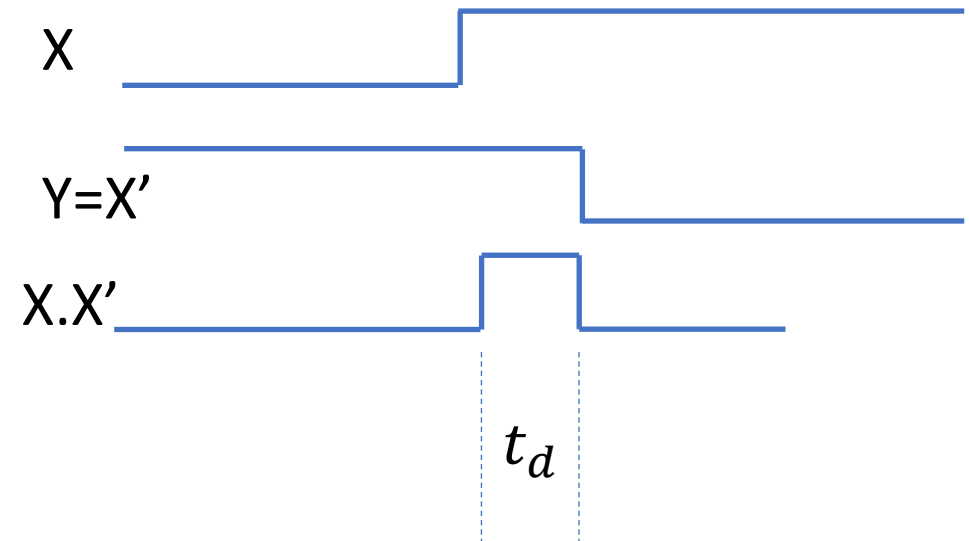
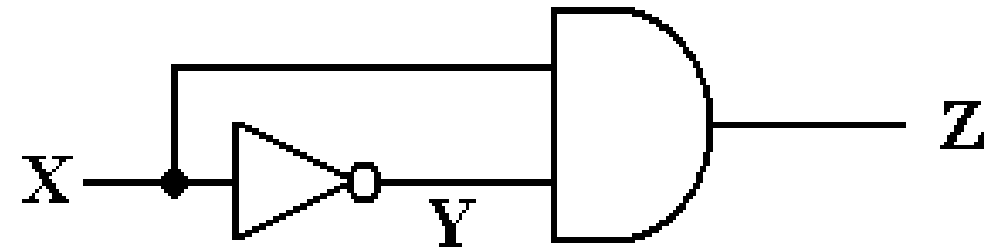
# Glitches

- Improperly handled timing can lead to glitches and cause unexpected results
- This is particularly true for multi-level logic implementation wherein different literals are bypassing some levels
- Consider an AND gate connected to  $X$  and  $X'$
- Such a connection will ALWAYS produce a glitch for  $X$  (0→1)


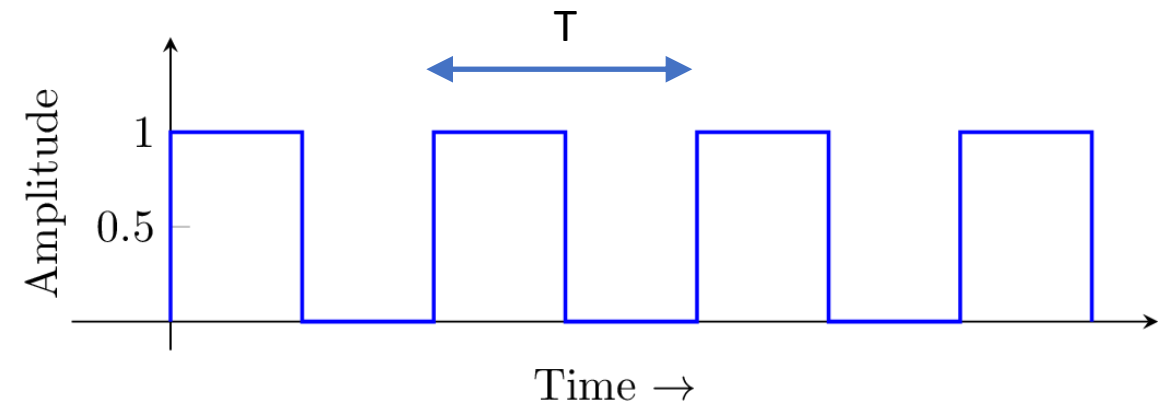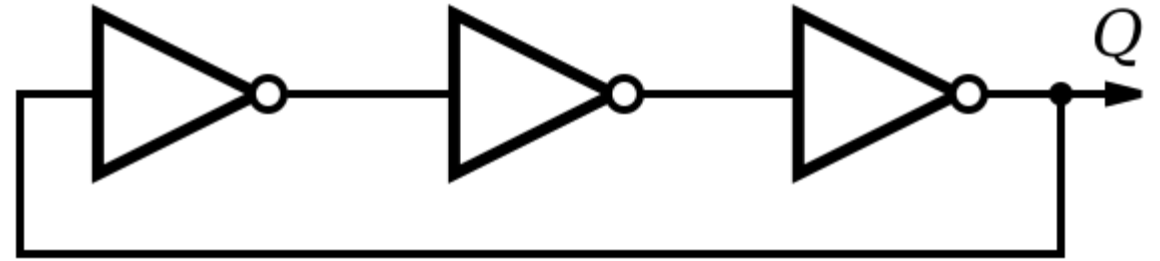
# Ring oscillators

- Another clever use of gate delays in is in the construction of **ring oscillators**
- It is a series of odd number of NOT gates with the output connected back to the input gate of the first gate
- With this system, we can generate a continuous square wave at Q
- What is the frequency of the wave?
- In this case, it is  $f = \frac{1}{T} = \frac{1}{3 \times 2t_d}$



# Sequential circuits

- The technology enabling and supporting modern digital devices is critically dependent on electronic components that can store information, i.e., have memory
- We will examine the operation and control of these devices and their use in circuits and enables you to better understand what is happening in these devices when you interact with them
- The digital circuits considered thus far have been combinational—their output depends only and immediately on their inputs—they have no memory, i.e., dependence on past values of their inputs
- Sequential circuits, however, act as storage elements and have memory, i.e., their output depends on past inputs as well

# Sequential circuits

- The main way sequential circuits remember things is through feedback paths and memory elements
- We know how combinational circuits are created
- The simplest storage elements (memory) used in sequential circuits are called *latches*

